



EnterMedSchool.org

Electricity: Ohm's Law and Capacitors

Exam — Electricity

Pre-med style questions on current, voltage, resistance, power, series/parallel circuits, meters, internal resistance, and capacitors ($Q=CV$, series/parallel, energy, dielectrics, and RC charging/discharging). Focused on conceptual traps and exam-style reasoning.

75 items — Printable Exam

Free & Open-Source

Licensed under Creative Commons — Attribution required when sharing

Generated February 20, 2026

Scan to visit online





1 Electric current is best defined as:

- A The total charge contained in a wire
- B The energy carried by electrons each second
- C The force pushing charges through a conductor
- D The rate of flow of electric charge
- E The resistance of a circuit to charge flow



2 In a metal wire connected to a battery, the direction of conventional current is:

- A The same direction as electron drift
- B Opposite to electron drift
- C Always from the negative terminal to the positive terminal in the external circuit
- D Random because electrons move randomly
- E Only within the battery, not in the wire



3 Potential difference (voltage) between two points is best interpreted as:

- A Charge per unit time
- B Energy transferred per unit charge
- C Force per unit charge
- D Energy transferred per unit time
- E Resistance per unit length





4 A battery has emf E and internal resistance r . When it delivers current to an external circuit, the terminal potential difference is typically:



- A Greater than E because current "boosts" the voltage
- B Equal to E for any current
- C Less than E because some energy per charge is lost inside the battery
- D Zero because voltage is used up in the battery
- E Negative because internal resistance reverses polarity

5 Ohm's law states that for an ohmic conductor:



- A Current is proportional to resistance
- B Voltage is proportional to resistance
- C Voltage is proportional to current, provided temperature (and other physical conditions) are constant
- D Power is proportional to current
- E Resistance is proportional to voltage for all materials

6 Which component is most likely to be approximately ohmic over a wide range of currents at constant temperature?



- A A filament lamp
- B A fixed metal resistor
- C A diode
- D An LED
- E A thermistor





7 A graph of voltage V (vertical axis) against current I (horizontal axis) for an ohmic resistor is a straight line through the origin. The slope of this line equals:



- A** $1/R$
- B** R
- C** Power
- D** Charge
- E** Capacitance

8 A graph of current I (vertical axis) against voltage V (horizontal axis) for an ohmic resistor is a straight line through the origin. The slope of this line equals:



- A** R
- B** $1/R$
- C** IR
- D** V/R^2
- E** Capacitance

9 A resistor stays at constant temperature. If the potential difference across it doubles, the current through it will:



- A** Halve
- B** Double
- C** Quadruple
- D** Stay the same





E Become zero

10 A uniform wire has resistance R . If its length is doubled (same material and cross-sectional area), its resistance becomes:



- A $R/2$
- B R
- C $2R$
- D $4R$
- E R^2

11 A uniform wire has resistance R . If its cross-sectional area is doubled (same material and length), its resistance becomes:



- A $2R$
- B R
- C $R/2$
- D $4R$
- E R^2

12 Which statement about resistivity is correct?



- A depends on the length of the conductor
- B depends on the cross-sectional area of the conductor





- C** is a property of the material (and temperature), not the object's shape
- D** is the same as resistance R
- E** is measured in ohms (Ω)

13 As the temperature of a typical metal wire increases, its resistance usually:



- A** Decreases because electrons move faster
- B** Increases because lattice vibrations cause more collisions
- C** Stays constant because resistance depends only on length
- D** Becomes zero
- E** Becomes negative

14 A filament lamp is connected to a battery. As the current increases, the filament heats up. Which best describes the lamp's I - V behavior?



- A** Linear: V is always proportional to I
- B** Nonlinear: resistance increases with current/temperature, so the slope V/I increases
- C** Nonlinear: resistance decreases with current/temperature, so the slope V/I decreases
- D** The current becomes independent of voltage
- E** The lamp becomes a perfect conductor at higher current

15 An NTC thermistor is a component whose resistance decreases when temperature increases. Which best explains why it is non-ohmic in typical use?





- A Because Ohm's law never applies to semiconductors
- B Because the resistance changes as current heats it, so V is not proportional to I under changing temperature
- C Because it has zero resistance at all temperatures
- D Because it only works in parallel circuits
- E Because current is not defined in thermistors

16 Two resistors are connected in series to a battery. Which statement is always true (ideal components)?



- A The voltage across each resistor is the same
- B The current through each resistor is the same
- C The power dissipated by each resistor is the same
- D The resistance of the combination is less than each resistor
- E The total current equals the sum of currents through each resistor

17 Two resistors R_1 and R_2 are connected in series. If $R_2 > R_1$, then the voltage drop across R_2 is:



- A Smaller than across R_1 because current chooses the easier path
- B Equal to across R_1 because series circuits share voltage equally
- C Greater than across R_1 because the same current flows and $V = IR$
- D Zero because the larger resistor blocks the circuit
- E Unpredictable without knowing the battery's internal resistance





18 Two resistors are connected in parallel to a battery. Which statement is always true (ideal components)?



- A The current through each resistor is the same
- B The voltage across each resistor is the same
- C The equivalent resistance is the sum of the resistances
- D The voltage across the combination is zero
- E The power dissipated by each resistor is equal

19 Which statement about equivalent resistance is correct?



- A Two resistors in series have an equivalent resistance smaller than either one
- B Two resistors in parallel have an equivalent resistance larger than either one
- C For two resistors in parallel, the equivalent resistance is less than the smaller resistor
- D Series and parallel give the same equivalent resistance
- E Equivalent resistance is always the average of the resistances

20 A circuit has a fixed battery voltage and a single resistor. If a second resistor is added in series, the total current drawn from the battery will:



- A Increase
- B Decrease
- C Stay the same
- D Become zero for any added resistor
- E Reverse direction





21 A circuit has a fixed battery voltage and a single resistor. If a second resistor is added in parallel, the total current drawn from the battery will:



- A** Decrease because current splits
- B** Increase because total equivalent resistance decreases
- C** Stay the same because voltage stays the same
- D** Become zero because parallel cancels resistance
- E** Become unpredictable

22 A single identical bulb is connected to an ideal battery. Then two identical bulbs are connected in series to the same battery. Compared with the single-bulb case, each bulb in series will be:



- A** Brighter
- B** Dimmer
- C** Same brightness
- D** Off (no current flows)
- E** Brightness cannot be compared without the bulb's color

23 A single identical bulb is connected to an ideal battery. Then two identical bulbs are connected in parallel to the same battery. Compared with the single-bulb case, each bulb in parallel will be:



- A** Brighter
- B** Dimmer
- C** Same brightness





- D Off because current splits
- E Alternating between bright and dim

24 Two resistors R1 and R2 are in series with a battery. Which resistor dissipates more power?



- A The smaller resistance always dissipates more power
- B The larger resistance always dissipates more power
- C They dissipate equal power in series
- D Power depends only on the battery voltage, so it's equal
- E Impossible to know without numerical values

25 Two resistors R1 and R2 are connected in parallel across the same ideal battery. Which resistor dissipates more power?



- A The larger resistance always dissipates more power
- B The smaller resistance always dissipates more power
- C They dissipate equal power in parallel
- D Power depends only on current, so it's equal
- E Impossible to know without numerical values

26 Which expression for electrical power is always valid for any circuit element?



- A $P = IV$





- B** $P = I/R$
- C** $P = V/R$
- D** $P = IR$
- E** $P = V^2I$

27 For a resistor that obeys Ohm's law, which expression for power dissipated in the resistor is correct?



- A** $P = V + I$
- B** $P = I^2R$
- C** $P = R/I^2$
- D** $P = V/R^2$
- E** $P = R^2/I$

28 For a resistor that obeys Ohm's law, which alternative expression for power is correct?



- A** $P = V^2/R$
- B** $P = V/R^2$
- C** $P = R/V^2$
- D** $P = V^2R$
- E** $P = (V/R)^2R^2$





29 A heater uses power P for a time t . The electrical energy transferred is:



- A $E = P/t$
- B $E = Pt$
- C $E = P^2t$
- D $E = It$
- E $E = V/t$

30 A fuse in a household circuit is designed to:



- A Increase current when needed
- B Measure voltage in parallel
- C Melt and break the circuit if current exceeds a safe value
- D Provide extra resistance to save energy
- E Store charge to smooth out voltage

31 Compared with a fuse, a circuit breaker has the advantage that it:



- A Works only for low voltages
- B Can be reset after tripping
- C Always allows more current before breaking
- D Stores electrical energy
- E Reduces the resistance of the circuit





32 A voltmeter should be connected:

- A In series with the component, with very low resistance
- B In parallel with the component, with very high resistance
- C In parallel with the component, with very low resistance
- D In series with the component, with very high resistance
- E Across the battery only, never across components



33 An ammeter should be connected:

- A In series with the component, with very low resistance
- B In parallel with the component, with very low resistance
- C In series with the component, with very high resistance
- D In parallel with the component, with very high resistance
- E Only across the battery terminals



34 If a voltmeter mistakenly had a LOW resistance and was connected in parallel across a resistor, what would be the main consequence?

- A It would measure the voltage more accurately
- B It would draw significant current and change the circuit's behavior (measurement error)
- C It would stop current in the whole circuit
- D The resistor would become ohmic
- E Voltage would become negative





35 If an ammeter mistakenly had a HIGH resistance and was placed in series, what would be the main consequence?

- A** It would increase current because resistance adds power
- B** It would greatly reduce the circuit current, making the measurement unrepresentative
- C** It would not affect current because series current is fixed
- D** It would reverse the current direction
- E** It would make the circuit parallel



36 A 'short circuit' is dangerous primarily because it:

- A** Increases resistance so much that devices stop working
- B** Creates a very large current that can cause overheating and fire
- C** Makes voltage negative
- D** Eliminates the need for fuses
- E** Stops all charge movement



37 An 'open circuit' means:

- A** The resistance is very small
- B** The current is maximum
- C** There is a break so no complete path for current (current is zero)
- D** The battery voltage becomes infinite
- E** The circuit becomes parallel





38 Kirchoff's junction rule states that at a junction (node):



- A** Voltage is the same in all branches
- B** Sum of currents entering equals sum of currents leaving
- C** Sum of resistances equals zero
- D** Current is the same in all branches
- E** Power is conserved in each component

39 Kirchoff's loop rule states that around any closed loop in a circuit:



- A** The sum of currents is zero
- B** The sum of resistances is zero
- C** The sum of potential differences (rises and drops) is zero
- D** The sum of powers is zero
- E** Voltage is always the same across all elements

40 Two resistors form a potential divider (series) connected to a battery. The output voltage is measured across the LOWER resistor R2. If R2 is increased (battery voltage fixed), the output voltage across R2 will:



- A** Increase
- B** Decrease
- C** Stay the same
- D** Become zero
- E** Become equal to the current





41 A potential divider has R_1 on top and R_2 on bottom. The output is taken across R_2 . If R_1 is increased while R_2 and the supply stay fixed, the output voltage across R_2 will:



- A** Increase
- B** Decrease
- C** Stay the same
- D** Become equal to the supply voltage
- E** Become negative

42 A battery has emf E and internal resistance r . Which statement is correct when the battery supplies a larger current to a load?



- A** Terminal voltage increases because more electrons leave the battery
- B** Terminal voltage decreases because the internal voltage drop Ir increases
- C** Terminal voltage stays equal to E always
- D** Emf decreases to conserve energy
- E** Internal resistance becomes zero

43 A battery is not connected to anything (open circuit). Ideally, the terminal potential difference measured across its terminals equals:



- A** 0
- B** Its emf
- C** Half its emf
- D** Negative emf





E Ir

44 Capacitance C is defined as:



A $C = V/Q$

B $C = Q/V$

C $C = IV$

D $C = IR$

E $C = V/I$

45 The SI unit of capacitance is the farad (F). One farad is equivalent to:



A $C \cdot V$

B V/C

C C/V

D J/C

E $N \cdot m$

46 For a capacitor with fixed capacitance C , if the charge on it doubles, the potential difference across it will:



A Halve

B Double





- C Quadruple
- D Stay the same
- E Become zero

47 For a capacitor connected to a fixed battery voltage V , if the capacitance doubles, the charge stored on the capacitor will:



- A Halve
- B Double
- C Quadruple
- D Stay the same
- E Become zero

48 A charged capacitor primarily stores energy in:



- A The motion of electrons through the capacitor
- B The electric field between its plates
- C The magnetic field inside the plates (only)
- D Heat in the dielectric (always)
- E The capacitor's resistance

49 Which expression gives the energy stored in a capacitor of capacitance C at potential difference V ?





- A $U = CV$
- B $U = (1/2)CV^2$
- C $U = IV$
- D $U = V^2/C$
- E $U = (1/2)C/V^2$

50 A capacitor remains at fixed capacitance C . If the voltage across it doubles, the stored energy becomes:



- A Twice as large
- B Four times as large
- C Half as large
- D One quarter as large
- E Unchanged

51 A capacitor stays connected to a battery so V is constant. If capacitance C doubles, the stored energy becomes:



- A Half as large
- B Twice as large
- C Four times as large
- D Unchanged
- E Zero





52 Two capacitors are connected in parallel to a battery. Which statement is correct?



- A The charge on each capacitor is the same
- B The voltage across each capacitor is the same
- C The equivalent capacitance is smaller than either capacitor
- D The current through each capacitor is constant forever
- E Parallel capacitors always reduce total stored energy

53 Two capacitors are connected in series. Which statement is correct (ideal capacitors)?



- A Each capacitor has the same voltage
- B Each capacitor stores the same charge magnitude
- C The equivalent capacitance is the sum of the capacitances
- D The equivalent capacitance is greater than each individual capacitance
- E No charge can exist on capacitors in series

54 Which statement about equivalent capacitance is correct?



- A Capacitors in series add directly: $C_{eq} = C_1 + C_2$
- B Capacitors in parallel add directly: $C_{eq} = C_1 + C_2$
- C Capacitors in parallel always reduce total capacitance
- D Capacitors in series always give C_{eq} larger than each capacitor
- E C_{eq} for series is always the average of C_1 and C_2





55 Two identical capacitors each of capacitance C are connected in series. Their equivalent capacitance is:



- A $2C$
- B C
- C $C/2$
- D C^2
- E 0

56 Two identical capacitors each of capacitance C are connected in parallel. Their equivalent capacitance is:



- A $C/2$
- B C
- C $2C$
- D C^2
- E 0

57 For a parallel-plate capacitor, capacitance increases if you:



- A Decrease the plate area
- B Increase the plate separation
- C Increase the plate area
- D Remove charge from the plates
- E Decrease the battery voltage





58 For a parallel-plate capacitor, capacitance decreases if you:



- A** Decrease the plate separation
- B** Increase the plate separation
- C** Insert a dielectric
- D** Increase the plate area
- E** Increase the charge on the plates

59 Inserting a dielectric between capacitor plates (without changing geometry) generally causes the capacitance to:



- A** Decrease
- B** Increase
- C** Stay the same
- D** Become zero
- E** Become negative

60 An uncharged capacitor is connected to a DC battery through a resistor. Immediately after connection ($t = 0+$), the capacitor behaves most like:



- A** An open circuit (no current)
- B** A short circuit (very low voltage across it initially)
- C** A constant current source
- D** A diode





E A fuse

61 In the same RC charging circuit, after a long time (steady state with DC), the capacitor behaves most like:



- A A short circuit
- B A resistor of value R
- C An open circuit (no current through it)
- D A current source
- E A transformer

62 The time constant of an RC circuit is:



- A $= R/C$
- B $= RC$
- C $= C/R$
- D $= R + C$
- E $= 1/(RC)$

63 The SI unit of the RC time constant $= RC$ is:



- A Ohm (Ω)
- B Farad (F)





- C Second (s)
- D Volt (V)
- E Watt (W)

64 In an RC charging circuit, after one time constant $= RC$, the capacitor voltage V_c is approximately:



- A 0% of the final battery voltage
- B 37% of the final battery voltage
- C 50% of the final battery voltage
- D 63% of the final battery voltage
- E 100% of the final battery voltage

65 In an RC charging circuit, after one time constant , the current has fallen to approximately:



- A 0% of its initial value
- B 37% of its initial value
- C 50% of its initial value
- D 63% of its initial value
- E 100% of its initial value





66 If resistance R in an RC circuit is doubled while capacitance C stays the same, the time constant becomes:



- A Half as large
- B Twice as large
- C Four times as large
- D Unchanged
- E Zero

67 If capacitance C in an RC circuit is doubled while resistance R stays the same, the time constant becomes:



- A Half as large
- B Twice as large
- C Four times as large
- D Unchanged
- E Zero

68 An uncharged capacitor is charged from an ideal battery through a resistor R . Which statement about the INITIAL charging current ($t = 0+$) is correct?



- A It depends on the capacitance C : larger C gives larger initial current
- B It depends on the capacitance C : larger C gives smaller initial current
- C It is approximately V/R and does not depend on C
- D It is zero because capacitors block DC
- E It is infinite because the capacitor is a short circuit forever





69 A capacitor initially charged to voltage V_0 discharges through a resistor R . After one time constant $\tau = RC$, the capacitor voltage is approximately:



- A 0% of V_0
- B 37% of V_0
- C 50% of V_0
- D 63% of V_0
- E 100% of V_0

70 When a charged capacitor discharges through a resistor, the energy originally stored in the capacitor is mainly converted into:



- A Gravitational potential energy
- B Kinetic energy of the capacitor plates
- C Heat in the resistor (thermal energy)
- D Extra electric charge created from nothing
- E Mass of the electrons

71 A capacitor is charged from an ideal battery of voltage V through a resistor until fully charged. (Ideal components.) Compared to the total energy supplied by the battery, the energy finally stored in the capacitor is:



- A All of it (100%)
- B About half of it; the other half is dissipated as heat in the resistor
- C About a quarter of it
- D Zero; no energy is stored in a capacitor





- E More than the battery supplied (energy gain)

72 A capacitor remains connected to a battery (constant V). A dielectric is inserted fully between the plates. What happens?



- A Capacitance decreases, charge decreases, stored energy decreases
- B Capacitance increases, voltage increases, charge stays the same
- C Capacitance increases, voltage stays the same, charge increases
- D Capacitance increases, charge stays the same, voltage increases
- E Nothing changes because the battery fixes everything

73 A charged capacitor is isolated (disconnected from any battery) so its charge Q is fixed. A dielectric is inserted fully between the plates. What happens?



- A Capacitance increases, voltage decreases, stored energy decreases
- B Capacitance increases, voltage increases, stored energy increases
- C Capacitance decreases, voltage decreases, stored energy decreases
- D Capacitance stays the same because it is isolated
- E Charge becomes zero instantly

74 A capacitor C is charged to voltage V and then disconnected from the battery. It is then connected in parallel to an identical uncharged capacitor. Which statement is correct (ideal wires, no battery)?



- A Final voltage remains V and total stored energy stays the same





- B** Final voltage becomes $V/2$ and some energy is dissipated (e.g., as heat/radiation) during charge redistribution
- C** Final voltage becomes $2V$ because charge doubles
- D** Final voltage becomes zero because charge cancels
- E** Charge is not conserved in capacitors, so nothing can be predicted

75 Why can a capacitor help smooth the output of a rectifier (reducing ripple in a DC supply)?



- A** Because it permanently increases the battery voltage
- B** Because it converts AC directly into DC without losses
- C** Because it stores charge when voltage is high and releases charge when voltage drops, reducing fluctuations
- D** Because it blocks all current so the output becomes constant
- E** Because capacitance decreases when voltage changes







#	Ans	Answer Text
1	D	The rate of flow of electric charge
2	B	Opposite to electron drift
3	B	Energy transferred per unit charge
4	C	Less than E because some energy per charge is lost inside the battery
5	C	Voltage is proportional to current, provided temperature (and other phys...
6	B	A fixed metal resistor
7	B	R
8	B	1/R
9	B	Double
10	C	2R
11	C	R/2
12	C	is a property of the material (and temperature), not the object's shap...
13	B	Increases because lattice vibrations cause more collisions
14	B	Nonlinear: resistance increases with current/temperature, so the slope V...
15	B	Because the resistance changes as current heats it, so V is not proporti...
16	B	The current through each resistor is the same
17	C	Greater than across R1 because the same current flows and $V = IR$
18	B	The voltage across each resistor is the same
19	C	For two resistors in parallel, the equivalent resistance is less than th...
20	B	Decrease
21	B	Increase because total equivalent resistance decreases
22	B	Dimmer
23	C	Same brightness
24	B	The larger resistance always dissipates more power
25	B	The smaller resistance always dissipates more power
26	A	$P = IV$
27	B	$P = I^2R$
28	A	$P = V^2/R$
29	B	$E = Pt$
30	C	Melt and break the circuit if current exceeds a safe value
31	B	Can be reset after tripping
32	B	In parallel with the component, with very high resistance
33	A	In series with the component, with very low resistance
34	B	It would draw significant current and change the circuit's behavior (mea...
35	B	It would greatly reduce the circuit current, making the measurement unre...
36	B	Creates a very large current that can cause overheating and fire
37	C	There is a break so no complete path for current (current is zero)
38	B	Sum of currents entering equals sum of currents leaving



